

Nevermind...

↳ Need to think of these as two separate state machines
↳ Cut #1 down to 3 states

#1 : X

EN	Q_1	Q_2	Q_1^+	Q_2^+	X	Y	Z
0	0	0	0	1	0	0	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
1	X	X	X	X	0	0	0

X's because it would be redundant for the states AND output to be determined by EN. Could have it set to 00 but would already have to tailor XYZ anyways

XYZ \equiv decoder with EN'

$$Q_1^+ = Q_2, \quad Q_2^+ = Q_1' \cdot Q_2'$$

#2: 0

EN	Q_1	Q_2	Q_1^+	Q_2^+	A	B	C	D
1	0	0	0	1	0	0	0	1
1	0	1	1	0	0	0	1	1
1	1	0	1	1	0	1	1	1
1	1	1	0	0	1	1	1	1
0	X	X	X	X	0	0	0	0

$$Q_1^+ = Q_1 \oplus Q_2, \quad Q_2^+ = Q_2'$$

Q_1, Q_2	A	B	C	D
00	0	0	0	1
01	0	0	1	1
10	0	1	1	1
11	1	1	1	1


$$D = EN$$

$$C = (Q_1 + Q_2) \cdot EN$$

$$B = Q_1 \cdot EN$$

$$A = (Q_1 \cdot Q_2) \cdot EN$$

#1 Circuit

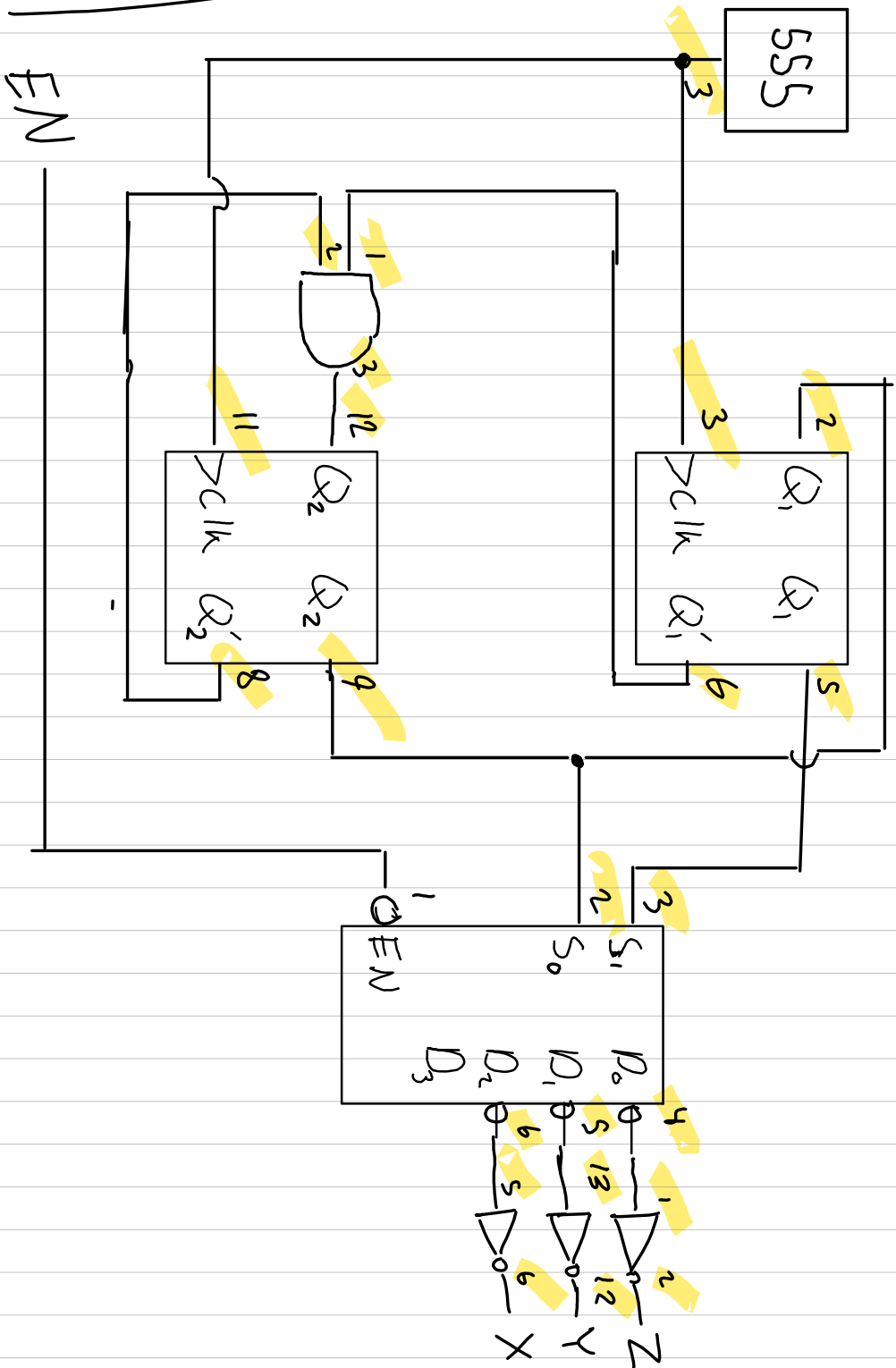

#2 Circuit

